


# IC Design

## Homework # 4

(Due on 2020/01/03, 14:00, Verilog code and report upload to CEIBA, no hardcopy)


- ✧ Plagiarism is not allowed. 10% penalty for each day of delay.
- ✧ (Ex: Before 2020/01/04, 13:59, 10% penalty.)
- ✧ Any further questions, you can leave messages on the board of the class website or send e-mail to the TA.

### Specifications

 


$$D = BC \cos \angle A = \frac{B^2 + C^2 - A^2}{2}$$

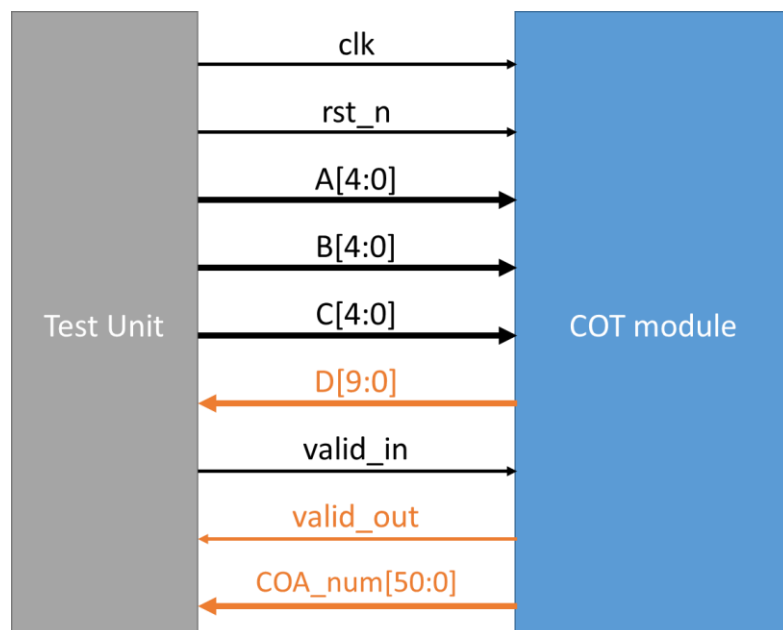Design a calculation circuit with reset that computes the **Cosine of an Angle**. There are three inputs, i.e., A with 5 bits, B with 5 bits, and C with 5 bits. And there is one output D with 10 bits. Note that all the inputs and output are **unsigned integers**. The relation between input and output is




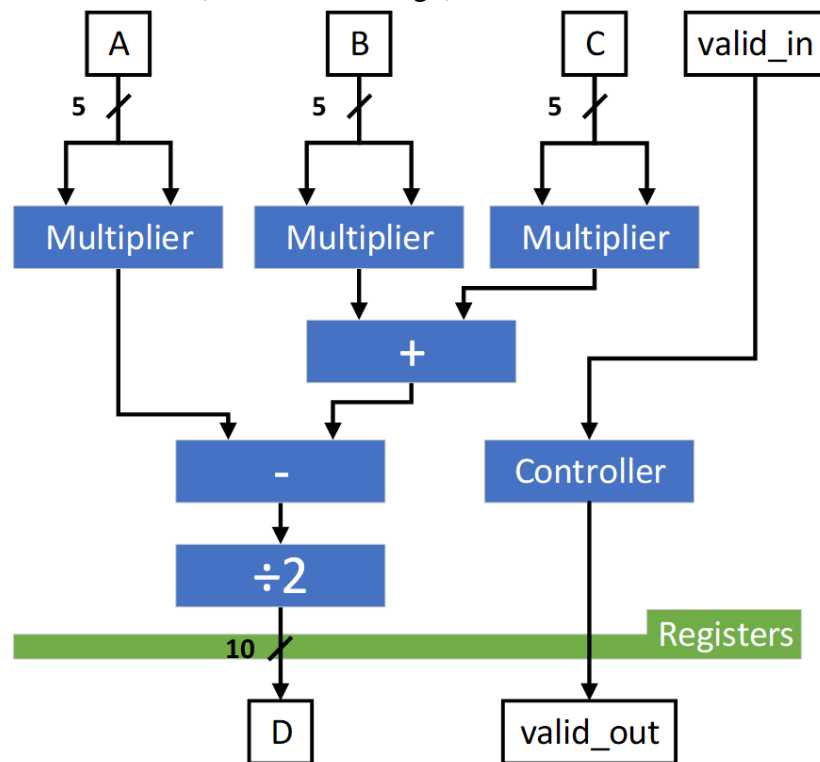Note that the two output signals: “D[9:0]” and “valid\_out” must be registered, i.e., they are outputs of DFFs (**use module FD2 (positive edge) in lib.v**). A possible architecture is as follows (not the best design):


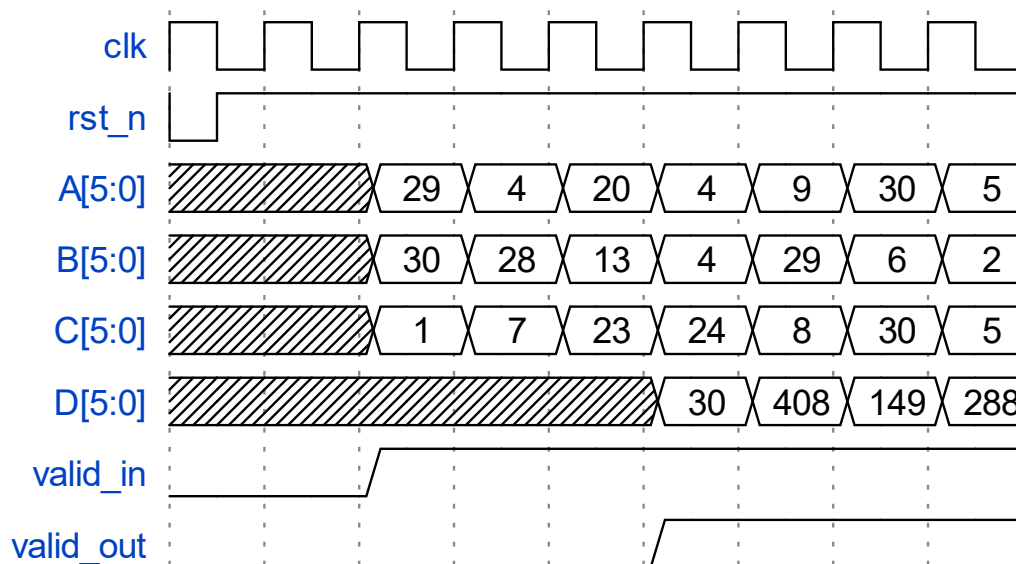
### COA Timing Diagram

The following figure is a possible timing diagram of the pipeline architecture. After a certain delay time, the COA module will continue to output results.



### Handshake signals

Signal name	I/O	Simple description
valid_in	Input	When valid_in == 1, Test_Unit will send a set of data (A, B, C) to the COA module.
valid_out	Output	The COA module needs to generate “valid_out” by itself. Once valid_out == 1, Test_Unit treats the data (D) as valid and starts receiving data (D).

### Data truncation

Since you need to divide by 2 at the end, you need to truncate the data to 10-bit. Here are some examples.

Signal	Value	
A	29	4
B	30	28
C	1	7
$A^2$	841	16
$B^2$	900	784
$C^2$	1	49
$B^2 + C^2 - A^2$	60	817
D[10:0]	30	408.5
D[9:0]	30	408

### Design Rules

- **Those who do not design according to the following rules will not be graded.**
- There should be a **reset signal** for the register.
- You may need to add pipeline registers to speed up design.
- You can loosen your simulation timing first, (i.e., ``define HALF_CYCLE XXXX` in the testbench.v), then shorten the clock period to find your critical path.
- Your design should be based on the **standard cells in the lib.v**. All logic operations in your design **MUST consist of the standard cells** instead of using the operands such as “+”, “-”, “&”, “|”, “>”, and “<”.
- Design your homework in the given “COA.v” file. **You are NOT ALLOWED to change the filename and the header of the top module (i.e. the module name and the I/O ports).**
- If your design contains more than one module, **don’t create new file for them**, just put those modules in “COA.v.”

## Grading Policy

### 1. Gate-level design using Verilog (70%)

Your score will depend on both the correctness and performance of your design.

#### (a) Correctness Score (40%)

At this stage, we will only evaluate whether the function of the COA module is correct. Time and area are not considered. We provide a test bench with 1000 patterns which automatically grades your design. Your score in this part will be

$$40 \times \frac{\text{correct number}}{1000}$$

#### (b) Performance Score (30%)

At this stage, you need to add up the number of transistors of all used cells in the COA module and connect it to COA\_num[50:0].

Only in this section, you are allowed to use “assign” and “+” to help calculations.

(i.e., **assign COA\_num = AD3\_N + AN4\_N;**)

We will rank all students who pass (a) and have **no connection errors on COA\_num**. There will be a ranking according to **AT**, where A represents the **number of transistors** and T represents the **execution time**. Your performance score will be according to your ranking as the table below.

Percentage of passing students	Performance Score
If your ranking > 90 %	30
80% ~ 90%	27
70% ~ 80%	24
60% ~ 70%	21
50% ~ 60%	18
40% ~ 50%	15
30% ~ 40%	12
20% ~ 30%	9
10% ~ 20%	6
0% ~ 10%	3
Using operands, not standard cell logic	0
Correctness failed	0
Plagiarism	0

## 2. Report (30%)

### (a) Simulation (0%)

Write down your minimum half-cycle time. **If you do not provide this information, “1. Gate-level design using Verilog (70%)” will not get any score.**

**This minimum half-cycle time would be verified by TAs.**

### (c) Circuit diagram (10%)

You are encouraged to use software to help draw architecture **instead of hand drawing**. Plot it **hierarchically** so that readers can understand your design easily. **All of the above will improve your report score.**

(5%) Plot the gate-level circuit diagram of your design **using a drawing tool instead of by hand**.

(5%) Plot critical path on the diagram above.

### (c) Discussion (20%)

Discuss about your design.

- (3%) Introduce your design.
- (2%) How do you cut your pipeline?
- (5%) How do you improve your critical path and the number of transistors?
- (5%) How do you trade off between area and speed?
- (5%) Compare with other architectures you have designed (if any).

## Notification

Following are the files you will need (available on the class website)

HW4.zip includes

- **HW4\_2019.pdf:** This document.
- **HW4\_tutorial\_2019.pdf:** Tutorial in class.
- **COA.v:**

Dummy design file. Program the design in this file.

The header of the top module and the declaration of the I/O ports are predefined in this file and you are not allowed to change them.

- **lib.v:** Standard cells.

- **testbench.v:**

Test bench for your design.

- **A.dat, B.dat , C.dat:**

Input patterns for test bench. Please put these files in the folder that contains testbench.v when doing simulation.


- **answer.dat:**

Output patterns of correct answers for test bench. Please put the file in the folder that contains testbench.v when doing simulation.
 
## Submit files

All students who do not submit files according to the rules **will get 20% penalty.**

- You should upload a **zip file** to **CEIBA**, the file name is “HW4\_Student ID\_vx”, vx represents the version you submitted. Ex: HW4\_b06901001\_v1.zip
- Your file must conform to the following structure.



## Testbench description

- The output waveform will be dumped to file “COA.fsdb”, you can use nWave to examine it.
- You can change the number of test data to debug, but the final score will still test 1000 sets of data. (**``define N 1000`**)
- You can enable the debug function, which will display the data sent and received. (**``define debug 0`**)

TA email: [r07943012@ntu.edu.tw](mailto:r07943012@ntu.edu.tw), EE2-329

HW4 Office hours: 2019/12/30 (Mon) 19:00~21:00 @BL212

2019/01/02 (Thus) 19:00~21:00 @BL211

If you have no time at office hours, you can email TA to discuss another time for appointment.